



Electronic
TUBE

Ham News

Copyright 1952, by General Electric Company

MARCH—APRIL 1952

VOL. 7—NO. 2



OSCILLATOR-MONITOR

Phone—CW Monitor and Code Practice Oscillator
for Novice or Oldtimer

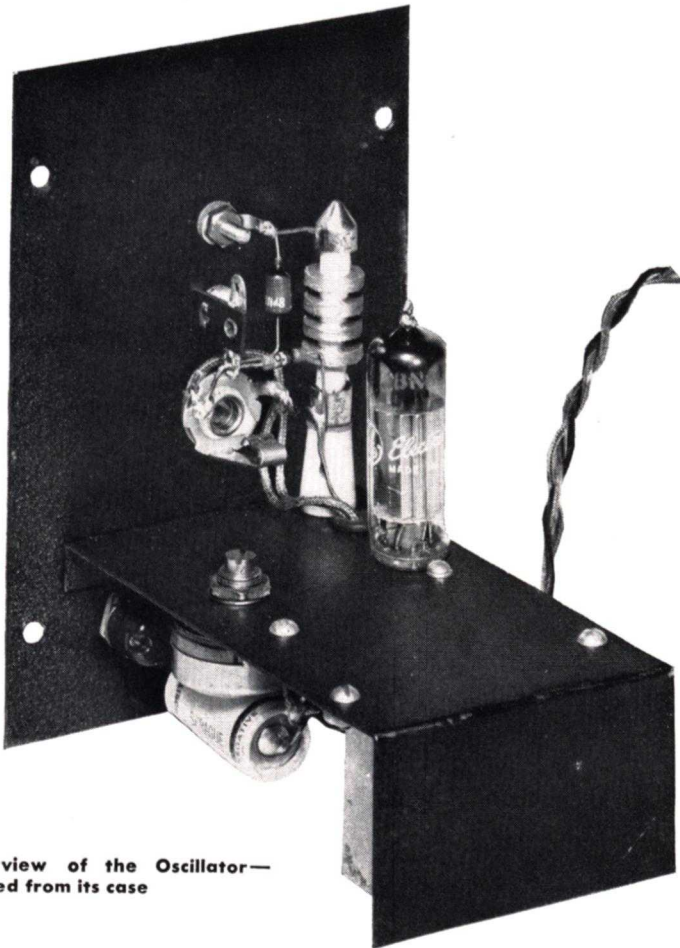


Fig. 1. Rear view of the Oscillator—
Monitor removed from its case

Contents

Oscillator—Monitor.....	pages 1-4
Tricks & Topics.....	page 5
Designer's Corner.....	page 6
Sweeping the Spectrum.....	page 7
Technical Information (1N4B).....	page 8

The cathode bias resistor, R_3 , is mounted on the chassis and is provided with a screwdriver slot for adjustment. Once this control is set no further changes are required in the setting unless another tube is used. Fig. 1 shows how the r.f. part of the circuit is mounted above the chassis. All other parts are mounted under the chassis. A hole must be provided in the rear of the cabinet to pass the three-wire power cable.

The antenna post and the keying jack must be insulated from the front panel. This may be accomplished with fiber washers. The output jack does not require insulation, but make certain that condenser C_4 connects to the ungrounded terminal of this jack.

The germanium diode, G , is connected as indicated. Most diodes are marked with a line around one end. This end is the cathode end, and should connect to R_1 , as the circuit diagram indicates.

Transformer T is a standard universal output transformer. The secondary is not used. The primary is connected as indicated, using the push-pull connection, with one plate end going to pin 5, the other plate end going to C_2 , and C_3 and R_4 connected from the center-tap to the plate end which connects to pin 5.

In the circuit diagram you will note that a maximum voltage of 85 volts may exist at the junction of R_5 and R_6 . This is very important. If too much voltage is applied to grid 2, the tube will not operate in the intended manner, and it may be damaged. Resistor R_6 is intended to drop the voltage to approximately 80 volts when 300 volts is applied externally. If you intend to use an external source of voltage which is lower than 300 volts, then R_6 may be made smaller. For example, if you use 100 volts, R_6 could be 1500 ohms. Whatever the external voltage may be, use a value for R_6 which will reduce the voltage on the other side of R_6 to at least 85 volts, and you may go as low as 50 volts at this point if you wish.

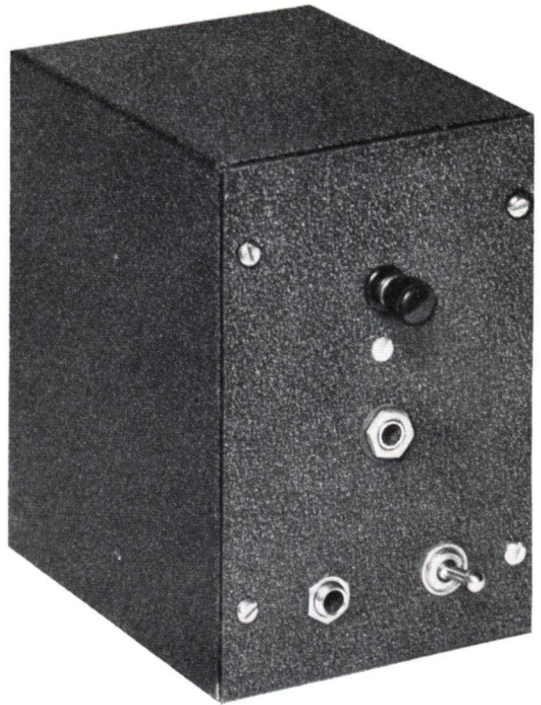


Fig. 3. Front view of the Oscillator-Monitor

CIRCUIT CONSTANTS

(All resistors and capacitors = 20% tolerance unless specified otherwise)

C_1	10 mf 50 volt electrolytic (Sprague TA 510)
C_2	1000 mmf mica or ceramic or paper
C_3	6000 mmf mica (see text)
C_4	0.05 mf paper
G	Crystal diode (G-E 1N48)
J_1, J_2	Open-circuit phone jack
R_1, R_5	0.1 megohm, $\frac{1}{2}$ watt
R_2	0.47 megohm, $\frac{1}{2}$ watt
R_3	500 ohm potentiometer
R_4	33,000 ohm, $\frac{1}{2}$ watt (see text)
R_6	22,000 ohm, 2 watt (see text)
RFC.....	2.5 mh r-f choke (Millen No. 34100)
S	SPST toggle switch
T	Universal output transformer (Stancor A-3823)

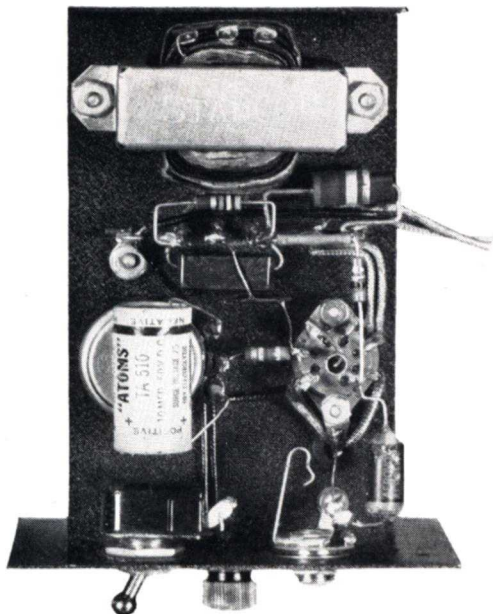


Fig. 4. Under-chassis view of the Oscillator-Monitor

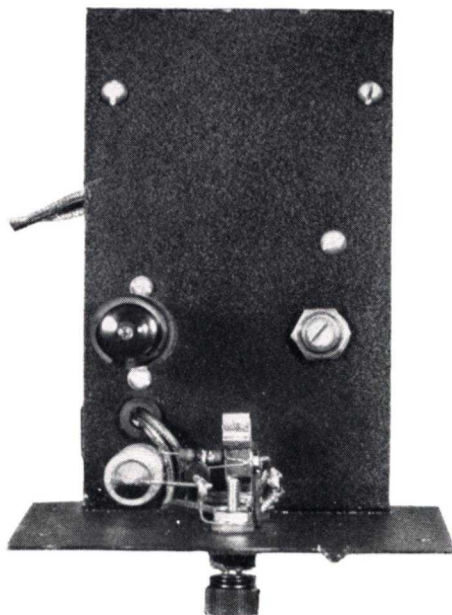


Fig. 5. Top-chassis view of the Oscillator-Monitor

TUNE-UP ADJUSTMENTS

After the unit is completed, connect 6.3 volts a.c. between ground and the filament connection wire. Next, connect the high voltage with the negative connection to ground and the positive connection to the lead marked 80-300 volts. Make certain that switch **S** is open (in the c.w. position).

Plug a key in the key jack and close the key. Insert a pair of earphones in the output jack, and listen for an audio note. Adjust R_3 until you get a good, clear note. Try the key to make certain that the note can be keyed.

If the note is the wrong tone, change the value of C_3 . A larger value will give a lower tone, and a smaller value will give a higher tone. The value specified will produce a satisfactory tone with the transformer specified, but if another type of transformer is used, it may be necessary to change the value of C_3 until a pleasing tone is obtained.

If you do not obtain a tone with the key closed, change the value of R_4 to a higher value, say 50,000 ohms. If you obtain a tone regardless of whether the key is closed or not, change R_4 to a lower value, and keep decreasing the value of R_4 until the tone no longer appears when the key is open.

The unit should now be in operating order. To check the operation as a monitor, place an antenna on the antenna post. This may be a piece of wire whose length depends upon the power of the transmitter being monitored. If you are using a low-power transmitter, you may need to run the wire near the antenna feedline in order to get enough energy to trigger the unit. Do not use any more wire for an antenna than is absolutely necessary because it is possible to overload the monitor. When the monitor is overloaded it will not oscillate. When you have the proper amount of pickup, an audio note will appear in the earphones when you key the transmitter.

If the transmitter does not seem to trigger the unit, you may have the germanium diode connected in backwards. Reverse the connections in this case.

In order to make the unit more sensitive to r.f. signals, the r.f. choke may be replaced with a tuned circuit. Generally this will not be necessary, and the circuit as shown should work on almost any amateur band.

For 'phone monitoring you may test the unit by modulating your transmitter, and checking to see if the voice is heard. Switch **S** must be closed for 'phone monitoring. If you live close to a local broadcasting station you may find that you will hear this station. This is to be expected, because the monitor is working as a monitor for the local broadcast station. If the station is loud enough to be troublesome, you may have to put a wavetrap in the antenna circuit.

USING THE OSCILLATOR-MONITOR

When used as a 'phone monitor, earphones must be employed. However, when the unit is used as a keying monitor the earphones may be replaced with a small speaker and matching transformer. A universal output transformer with its primary connected to the output jack will serve nicely. It is also possible to feed the output of the monitor directly into the audio input of the receiver in use, and thus take advantage of the audio amplifier and speaker in the receiver. In this way the received signal will be heard on the receiver when you are in contact with some amateur, and your own signal will be fed into the receiver through the monitor when you are transmitting. No switching is required, although some means must be used to make the receiver insensitive to your own transmitted signal.

How did you solve that last problem that almost had you stumped? Be it about tubes, antennas, circuits, etc., Lighthouse Larry would like to tell the rest of the hams about it. Send it in! For each "trick" published you win \$10 worth of G-E Electronic Tubes. Mark your letter "Entry for Tricks and Topics" and send to Lighthouse Larry Tube Division, Bldg. 269, General Electric Company, Schenectady, New York, or in Canada to Canadian General Electric Company, Ltd., Toronto, Ontario. The Companies shall have the right, without obligation beyond the above, to publish and use any material submitted to this column. No entries returned.

OLD TUBES AS BLEEDERS

Out-of-date transmitting triodes, or extra surplus-purchased triodes can be made to serve quite easily as high wattage bleeder resistors. A tube with a plate dissipation of fifty watts can be used as a fifty-watt bleeder resistor, for example.

Such tubes may be used as follows. Connect the filament center-tap to a self-bias resistor and thence to B minus. Connect the anode to B plus, and the grid to B minus. Use a spare filament transformer to supply the normal filament voltage.

The value of the resistor should be such as to permit the desired bleeder current to be drawn when the power supply is operating. This current times the power-supply voltage should not exceed the dissipation rating of the tube.

For example, a GL-203-A tube has a plate dissipation of 100 watts (the maximum CCS dissipation rating). If used as a bleeder on a 1000-volt power supply, a 50-ohm, 2-watt resistor will provide a bias of approximately minus 5 volts, and a current of 100 mills will flow. This is the maximum current which may be drawn and still keep the tube within the dissipation rating at 1000 volts. A larger value of resistance may be used if a lower current is desirable.

When the tube characteristics are unknown, the value of the bias resistor may be determined experimentally. Be sure to provide a resistor of sufficient power rating so that the bleeder current squared times the resistance is well within the resistor wattage rating.—W2KUJ

HOMEMADE TOOL FOR TWINLEAD

A very handy cutting and stripping tool for twin-lead can be made from a pair of old scissors. Refer to Fig. 6. Procure a pair of old household scissors, or an inexpensive pair of children's scissors. About one inch from the pivot point file or grind a V in each blade, so that when the blades are closed a little bit of light can be seen through the blades. Next, enlarge this area with a file or drill until you have a hole which is slightly larger than the diameter of the twin-lead wire. Now, file or grind a slight angle on the sides of the V's to form a good cutting edge. Finally, grind off the end of the scissors so that there is about one-half inch of blade from the center of the V's to the end of the blades.

The portion of the scissors from the V back to the pivot is normally used to cut the twinlead, and the front portion is used, with the V itself, to cut the internal portion of the insulation and to strip the

wire. The hole at the middle of the V portion straddles the wire and acts as the stripper.—W8TIC

MICROPHONE JACK SHIELD

Here is a simple and economical way to completely shield the microphone input jack on speech amplifiers. Procure one of the small aluminum screw-top cans in which each 35 mm. camera-film cartridge comes packed. Place the cap on a flat surface and with a small hammer, from the inside, pound out the small dome so that the top is flat. Then, drill a hole in the center of the cap and mount it directly on the rear of the microphone connector. If desired, a small hole can be punched with an icepick in the side of the cap near the top to permit the exit of a ground lead. If this is done, be sure the hole is above the threads.

Finally, cut a hole in the center of the bottom of the can, insert a rubber grommet, and you are finished. Plenty of room is provided inside the can for the grid resistor, and the bottom is easily unscrewed when access is desired.

The best way to make the holes in this thin aluminum stock and avoid jagged edges is to first drill a small hole and then enlarge it with a rat-tail file.—W9TUI

CHASSIS LAYOUT TRICK

Here is a trick that I think will save you time when you do that next layout job. Procure some cross-section paper (graph paper) from a stationery

store, and fasten this paper to the bare chassis with transparent adhesive tape. Try to get the type of graph paper that is divided by inches and tenths of inches.

The uniform markings on the paper act as a guide so that you can get a uniform layout. Also, you can visualize the size of the space occupied by various components, and avoid a crowded layout. The paper also protects the chassis from fingermarks and oil from your tools.—W1RQC

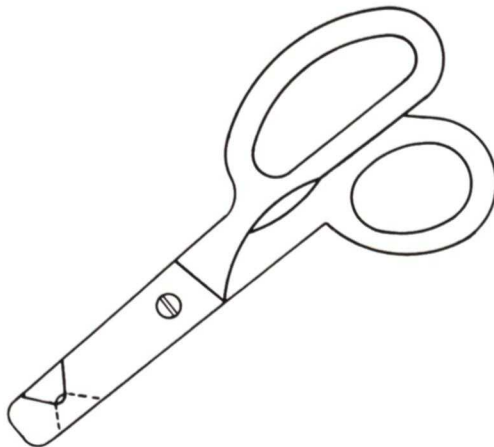


Fig. 6. Scissors arranged as per suggestion of W8TIC

Notes on Designing a Power Supply

This is not intended to be a deep technical discussion, but merely a clear, easy-to-follow description of how to select the right components for a power supply. For the reasons behind the statements about to be made you are referred to any amateur handbook. A power supply circuit is relatively simple, but unless certain fundamental rules are observed, the results obtained will not always be satisfactory.

The first two questions to be answered are: 1) do I need exceptionally good regulation? and, 2) how much ripple voltage can I tolerate? Both of these questions can be answered simply if you know the use to which the power supply will be put.

You will need good regulation if the current drain from the power supply is variable; that is, subject to change while in use. Examples of this sort of service would be power supplied to a class-B modulator stage, to class-B linear amplifier stages, or to the stages in a c.w. transmitter, including the keyed stage. On the other hand, if you are supplying voltage to a buffer stage in a 'phone transmitter, then regulation is not too important, because the current drain will be constant.

The question on ripple is just as easy to answer. For any stage in a c.w. transmitter, 5% ripple can be tolerated. For any stage in the r.f. section of a 'phone rig, except the modulated stage, 5% ripple is satisfactory. However, for the modulated stage itself, the power supply should have 0.25% ripple, or less. The audio stages should similarly have less than 0.25% ripple applied to them, except for the class-B modulator, where 5% ripple is satisfactory. In the case of high-gain audio amplifiers, as low as 0.1% ripple is desirable. This figure of 0.1% ripple applies also to power supplies used with receivers.

The ripple requirement determines the filtering necessary. A one-section filter ordinarily is used to reduce the ripple to 5%, but it is not usually economical to try to get much more reduction than that with a one-section filter. Considering full-wave circuits, where the ripple frequency is 120 cycles, five-percent ripple will be obtained when the product of inductance (in henrys) and capacitance (in mfd) equals twenty. A choke input filter with a 10-henry choke and a 2 mfd condenser will give 5% ripple. To achieve further ripple reduction a multiple-section filter is usually employed. A two-section filter of this sort might consist of an input choke, a condenser, a second choke, and another condenser. For example, if you added another 10-henry choke and a 4-mfd condenser to the filter constants given above, the overall filtering action would reduce the ripple to less than 0.2 percent. (Most handbooks tell you how to compute the ripple for other combinations of L and C.)

The regulation of a power supply, that is, the relation between the output voltage at no load and at full load, is determined almost entirely by the inductance of the input choke. The *minimum* value of inductance at this point which prevents the d.c.

output voltage from rising above the average value of the a.c. voltage being rectified is called the *critical inductance*. Conservative design indicates the use of a choke having a value at least twice the critical inductance.

The critical inductance, in henrys, for 120 cycle ripple is determined by dividing the load resistance by 1000. For example, a load of 1000 volts at 40 mils (the bleeder current, or minimum current only) gives a load resistance of 25,000 ohms. In this case, an input choke of 50 henrys would give excellent regulation characteristics (twice the 25 henrys critical inductance).

If you find that this value of inductance is too great a drain on the pocketbook, a lower value can be used if the bleeder current is increased. For example, an 80 mil bleeder will result in a critical inductance of 12.5 henrys, so that a 25-henry choke would be desirable. Note that the input choke need have this high value of inductance only at the minimum (bleeder) current. Swinging chokes are widely used for this reason.

Check the value of the bleeder in your present power supply, and see if you have one which is drawing sufficient current!

At this point in your thinking you are ready to select components for your power supply. You select an input choke of the calculated value with sufficient current rating to handle both the bleeder current and the useful load current. Next, select a condenser to give the required reduction in ripple when used with the input choke already selected (choose these values to avoid resonance at the ripple frequency—your handbook gives details). A second section can be selected if ripple requirements demand it. The bleeder resistor is determined as mentioned in the previous paragraph.

Next, compute the voltage drop across the choke or chokes, and add to this the voltage drop across the rectifier tube. Now add the desired output voltage, and multiply by 1.1 to get the value of a.c. r.m.s. voltage required from center-tap to one side of the transformer. For example, if the load current is 200 mils, the bleeder current 40 mils, and desired output voltage 1000 volts, compute the drop across the chokes due to 240 mils current (say this is 24 volts), add tube drop (say 15 volts for mercury-vapor tubes), and you get 1039 volts. Multiply by 1.1 and you get 1143 volts. You therefore want a transformer with a secondary voltage rating of 1143-0-1143, and with a current rating of approximately 250 mils. This transformer will supply a d.c. output voltage of 1000 volts and a useful current of 200 mils, in the power supply you just calculated.

Some transformers are rated for *d.c. output voltage* rather than for a.c. voltage. In this case the transformer manufacturer has already calculated the d.c. output voltage from a typical filter system. Just make certain that you know how the transformer is rated before you use it.

— Lighthouse Larry

SWEEPING *the* **SPECTRUM**



I recently received a very nice letter from W9ONY, president of the Milwaukee Radio Amateurs' Club, in which Fred expressed his appreciation to G.E. for the film *And a Voice Shall Be Heard*. To quote him: "The membership was thrilled over it and it certainly presents a vital message to all." This film, prepared by The March of Time for G.E., gives the story of civil defense in Onondaga County, New York. The part of the radio amateur is very well presented.

If you would like to arrange to show this film to your local club, a copy may be borrowed from one of the eighteen G.E. film libraries throughout the country. You can get the address of the nearest library by writing to your local G.E. office, or, by dropping me a note. The running time is approximately 20 minutes, and the film is 16 mm. sound. If you think your local civil defense office would be interested, ask one of the officials to drop in at your showing—he might wish to arrange to borrow the film for a general civil defense meeting.



Have you seen any lampshades around your town? The type I'm talking about wouldn't be inside a house, but would be mounted outside on a steel pole in some clear area. If there aren't any lightbulbs inside these lampshades, then the chances are that they are special radiation detectors, made to determine quickly and accurately the position of an atomic bomb explosion.

These radiation lampshades have been designed by a group of people in Schenectady, many of them employed in General Electric Co. The Schenectady County Civil Defense authorities have already installed a complete system of these detectors in the County.

The lampshade determines the height at which a bomb has exploded and the position of ground zero—the point directly under the blast. The device is made of sheet metal, about a foot in diameter, smaller at the top than at the bottom, and is painted white inside and out. On the inside, numbered vertical lines and horizontal lines are painted. A pointed brass rod projects upward inside the lampshade.

During an actual bombing, intense heat radiation would scorch the inside painted surface in relation to the direction of the burst, forming an unscorched shadow of the vertical rod. The position of the shadow gives information as to direction and height of the bomb burst. Readings taken from several lampshades can be correlated to give exact information.

Why talk about lampshades? Well, it seems to me that a couple of ham mobile rigs would be the ideal way to get the information back to Control Center in a hurry, where the plotting can be accurately completed.



Speaking of red-hot temperatures, the engineers in the Schenectady vacuum-tube plant recently had a problem which electronics solved for them. In making ignitrons (a special type of heavy-duty rectifier) it is necessary to heat some of the tube parts to rather high temperatures. However, just any temperature won't do, and the exact temperature is important to tube quality.

The solution was found in a G-E electric eye unit, which controls the temperature of the glowing graphite crucibles as they are heated to a temperature of approximately 3500 degrees Fahrenheit. At this temperature the graphite is a dazzling white color. The control unit is able to maintain temperatures in this range with an accuracy of 15 degrees.

You'll probably never want to know the temperature of the anode in your final tubes, but if they are running in the red-hot to white-hot range, you could read and control this temperature by using this G-E device.



A news release that passed over my desk recently told of the completion of a number of radar picket posts that have been installed by G.E. for the U.S. Air Force. The location and number of these posts is secret, according to G-E officials, but some of the unclassified information is quite interesting.

These radar installations are capable of detecting aircraft at long range, and are now protecting the U.S. and Canada against sneak enemy air attack. Installations in the Arctic regions are housed in rubberized fabric "radomes," supported entirely by air pressure, and resembling huge pumpkins.

An estimated 400 men are required to operate each installation, on a 24-hour basis. Imagine what a ham could do with an arrangement of that sort, especially if it was designed for DX work! With 400 helpers, one ought to be able to work at least 100 countries in an afternoon. Of course, you'd have to call it a multiple-operator station!

It's a comforting thought to know that these radar installations are now at work protecting our borders—serving as the outposts of our civil defense organization. What are you doing for civil defense these days?

—Lighthouse Larry


GERMANIUM DIODE

GENERAL DESCRIPTION

The 1N48 is a general-purpose germanium diode which exhibits a medium back-resistance characteristic and has a medium inverse voltage rating. The Mounting Position Any

1N48 is designed for most low-current power-rectification applications such as isolation, clipping, switching, and meter rectification.

PHYSICAL DIMENSIONS

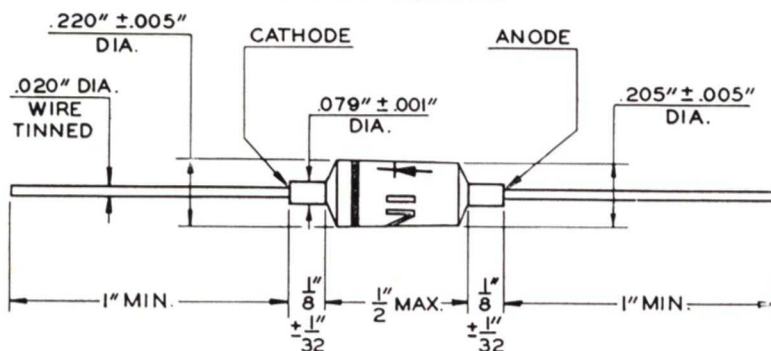

MAXIMUM RATINGS

AT AMBIENT TEMPERATURE OF +25 CENTIGRADE

Peak Inverse Voltage	85	Volts
Continuous Inverse Voltage	70	Volts
Average Rectified Current	50	Milliamperes
Peak Rectified Current	150	Milliamperes
Surge Current for 1 Second	400	Milliamperes
Ambient Temperature Range	-50 to +75	Centigrade



Ham News

Available FREE from

G-E Electronic Tube Distributors

Printed in U.S.A.

A Bi-monthly Publication

TUBE DEPARTMENT, ELECTRONICS DIVISION

GENERAL ELECTRIC

SCHENECTADY 5, N. Y.

(In Canada, Canadian General Electric Company, Ltd., Toronto, Ont.)

GEO. H. FLOYD, W2RYT—EDITOR

FROM: