

MOTOROLA**HEP**®**Semiconductors**

TIPS ON USING

**IC's**

- IC Cross-Reference Guide
- Eight IC Project Circuits
- Tips on Using IC's

8 PROJECTS

Build These 8 Projects Plus
Many Other Published Projects

With These Prime Quality,
Low Cost IC's.

- One J-K Flip Flop
- One 4-Input Gate
- One Dual Buffer
- Two Dual 2-Input Gates

Complete Schematic, Logic, and
Characteristics are Included.

IC'S ARE HERE TO STAY AND THE NEXT FEW YEARS WILL SHOW A MASSIVE TRANSITION IN INDUSTRY AND CONSUMER PRODUCTS TO COMPLETE INTEGRATION.

Based on this assumption, this brochure has been prepared for the novice as well as professional user of Integrated Circuits (IC's). It includes tips on wiring, soldering, cross referencing, and eight simple projects using the IC's contained in the Motorola HEP HEK-1 kit.

A lengthy discussion of IC construction will not be covered in detail, as this information can be found in many IC textbooks. However, in order to be better able to know the advantages and limitations of these microcircuits, the reader should know what is contained in the basic IC and how these devices differ from other solid state components.

As the name implies, an Integrated Circuit is a collection of many different components. The quantity and types of components vary from one IC configuration to another. A particular IC could contain ACTIVE components (transistors, diodes) and PASSIVE components (resistors, capacitors). If all the components of the circuit are contained on the same "CHIP" or substrate, the unit is said to be "MONOLITHIC" (single crystal). The monolithic type is the most common and the least expensive to build. Other construction types are: thin film, thick film, hybrid, multi-chip. A discussion of these types can be found in almost any book that deals with the subject of IC's.

As an illustration of the extreme size reduction possible with Integrated Circuits, consider the new Motorola 4-bit memory core, which contains 524 different components on a chip 50 mils x 70 mils. The average IC is much smaller, usually 40 mils square (1 mil = .001"). As the above example indicates, the race is on to see how much circuitry can be crowded into the smallest space. This effort is known in the trade as LSI (large scale integration). Manufacturers are already starting to produce IC's that contain FETS, tuning diodes, and even power transistors!

It is unfortunate, but many people are resisting the change-over from discrete (individual) components to IC's. This resistance could largely be due to the fact that people tend to shy away from circuits they are not familiar with.

The advantages of IC's over discrete components greatly outweigh the disadvantages. Size and weight reduction are obvious advantages but cost savings should also be considered. Refer to the schematic of the HEP 583, which contains 21 transistors and 27 resistors. If you had to buy all these parts individually and build this unit using a breadboard or printed circuit board you would indeed feel the pinch on both your pocketbook and your time. Other disadvantages that are not so obvious are as follows:

**MOTOROLA Semiconductor Products Inc.**

BOX 2953 • Phoenix, Arizona 85036 • Copyright © 1972, Motorola Inc.

www.SteamPoweredRadio.Com

REPETITION: If you need a circuit containing twenty J-K flip flops, it would be a difficult task to build 20 of these, each containing 21 transistors and 27 resistors. This adds up to 420 transistors and 540 resistors! With IC's, only 20 TO-5 packages are necessary. Here is where cost, size, and time advantages come through again.

REPEATABILITY: Because of the way IC's are constructed with components located in close proximity to each other, tolerances are much finer and parts are better matched, thus making up a device that functions as a complete unit. Power drain is lowered, there is less spurious noise pick-up, and there is less noise generated within the unit.

RELIABILITY: Many manufacturers are turning to IC's because of their high reliability. Devices built under almost clinical conditions are bound to be better than a circuit built on a work bench. Referring to an example given previously, consider that building the electrical equivalent to the HEP 583, using the 21 transistors and 27 resistors, it would be necessary to make 80 to 90 solder connections, a real source for potential trouble.

In addition to the advantages listed, replacement is simple. Schematics are easy to read, especially for the beginner. Areas yet to be conquered in the construction of IC's are: How to build inductors, large value capacitors, and high value resistance on an IC chip. It is presently necessary to connect these components externally.

GROUPS and SUBGROUPS

Broadly speaking, IC's can be divided into two categories, DIGITAL and LINEAR. IC's were born out of research for the space program where, for many years, their application was strictly in the field of DIGITAL work. ie, small computers on space craft where weight and power reductions were essential. Only in the last few years has the linear IC begun to blossom.

Table I shows some of the sub-groups to be found in IC's. The applications listed in Table I will be discussed later.

To further complicate matters, DIGITAL IC's are classified into logic families. The families and their construction are shown in table II.

TABLE I

LINEAR	DIGITAL
Differential Amps	Adders
Power Amps	Drivers
Audio Amps	Gates
Video Amps	Expanders
RF/IF Amps	Buffers
Operational Amps	Inverters
Sense Amps	Flip Flops

TABLE II

RTL	Resistor Transistor Logic
mW RTL	Low Power Resistor Transistor Logic
DTL	Diode Transistor Logic
VTL	Variable Threshold Logic
HTL	High Threshold Logic
ECL	Emitter Coupled Logic, also called Current Mode Logic
TTL	Transistor Transistor Logic — more than one emitter to device.
(NOTE: that VTL and HTL are forms of DTL)	

Table III shows the familiar characteristics of each line. Motorola manufactures complete lines in each family listed. To signify Motorola, you may see RTL written as MRTL, ECL as MECL, etc. A quick glance at Table III will

show that no one logic family has a clearcut advantage over any other family. For example, ECL is high frequency and internal noise immunity, where mW RTL has low power dissipation, etc.

TABLE III

Logic	Form	Delay Time	Freq. of Flip Flop (mHZ)	Power Dissipation (MW)	Noise Internal	Immunity Noise Ext
RTL	R _T	24	8	12	Fair	Fair
mW RTL	R _T	45	1 - 3	2.5	Fair	Fair
DTL	D _T	30	10	9	Fair	Good
VTL	D _T	50 - 60	1	12 - 80	Good	Excellent
ECL	Current Mode	6	30	35	Excellent	Fair
T ² T	T _T	10	20	15	Good	Good
HTL	D _T	200	3	45	Good	Excellent

MOUNTING IC's AND BREADBOARDING TECHNIQUES

IC's can be mounted on perforated board or printed circuit board by either soldering to terminals or by using sockets. Sockets are definitely recommended, especially for the hobbyist who will, generally, use the IC over and over in different applications. Constant soldering and unsoldering of the leads weaken them and could cause the wires to be broken, or internal damage could result due to excessive heat from the solder iron.

IC PACKAGING

Integrated circuits can be found in a variety of packages. At the present time, there are more than 120 case types made by some 70 companies around the world. Of these many case styles, three types are dominant. (In terms of quantity of devices on the market, in a given case type, about 90% of their quantity can be found in some variation of one of these three case types). As yet, no definite standardization has been set up among the manufacturers regarding packaging, pin numbers, and locations, so carefully check the basing before you plug that IC into the socket.

USE A LOW WATTAGE SOLDERING IRON! 25 to 40 watts is a good range. Excess heat could "kill" the IC.

The HEP 580 thru 583 (devices included in this IC kit) are mW RTL's. This logic family is considered the easiest for the hobbyist, experimenter, and IC novice to "cut their teeth" on.

The HEP 584, 570, 571, 572 are RTL's—also a good family for the beginner. The HEP 553, 554, 556, 558 are ECL's, — not the easiest to work with, but the best logic family for high frequency and noise rejection.


KEEP COMPONENT LEADS SHORT!

Excess lead length could cause spurious or parasitic oscillations or no operation at all.

If you are using a power supply, (other than a battery), it is a good idea to "bypass" the power leads. That is, connect a .05 or .1 mfd capacitor from the power input to ground at or near the input terminal of the IC.



TO-116

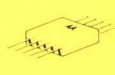

TO-91

TO-99 (8 PIN)
TO-100 (10 PIN)

POWER SUPPLIES

For projects using 1 or 2 IC's — batteries are usually the best supply. On larger projects, an a-c supply is better.


The power supply requirements for the various logic functions have been standardized and are, in general, as follows:

RTL	$3V \pm 10\%$ (2.6 to 3.3V) and $3.6 \pm 10\%$ (3.24 to 3.96V)
mWRTL	$3V \pm 10\%$ (2.6 to 3.3V) and $3.6 \pm 10\%$ (3.24 to 3.96V)
DTL	$4V \pm 10\%$ (3.6 to 4.4V)
MDTL	$5V \pm 10\%$ (4.5 - 5.5V)
VTL	$\pm 4V$ to $\pm 10V$ (8 - 20V)
ECL	$5.2V \pm 20\%$ (4.16 - 6.24V)
TTL	$5V \pm 10\%$ (4.5 - 5.5V)
HTL	18V

Obviously batteries in some of these odd voltage ranges are not available, however, experimentation has shown that on some lines the manufacturers are being much too conservative. For example in the HEP-580 series, many of the devices were found to work well from 1.5 to 12 volts! *Very few* did not — but after all, they are only rated from 2.6 to 4 volts (approximately). This makes it possible to use many of these IC's over a wide voltage range. Usually an IC rated at 3.2 volts minimum works well on 3 volts and one rated at 5.5 volts maximum, works at 6 volts.

IC's can be connected in one of two ways, using one or two supplies. The dual or split

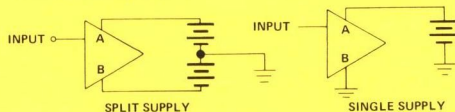supply is most common in linear circuits. (See follow example:)



There are some applications where the split or dual supply is advantageous but generally it involves more complicated circuitry.

The novice in IC's is likely to be a novice in the area of computer logic also. The logic symbols are to digital IC's what schematic symbols are to resistors, capacitors, etc.

Some of the more common types are shown below:




These symbols have recently been standardized by the government. Prior to that time, each manufacturer had his own set of symbols.

Most computers work on the binary principle. Binary stands for "two" — two states or conditions, which are either ON or OFF, (HIGH or LOW).

Consider the condition where we have zero or near zero volts at the input to a gate, flip-flop, amplifier, etc; it is an OFF condition. If this voltage goes positive, let's say, to 1 or 2

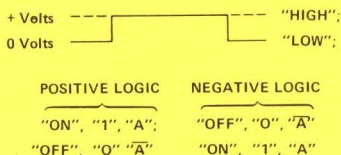volts it is now in an ON condition. There are two types of logic: Positive and negative. See below:



The common function in digital IC's are:

GATES — control the passage of signals.
BUFFERS (AMPLIFIERS) (DRIVERS) amplify power of signals to be able to drive more units.

INVERTERS — reverses the logic from + to — or — to +

EXPANDERS — affords additional inputs to a gate, example: allows 3-input gate to be converted to a 7-input gate.

ADDERS — provides the SUM and CARRY operations on two input signals.

SHIFT REGISTERS — provide bistable storage.

FLIP-FLOPS — Provides division or COUNT. One Flip-Flop divides by 2, provides 1 change in state output for 2 changes in state input.

From the standpoint of the hobbyist, only 3 functions are of interest; the Gate, the Amplifier, and the Flip-Flop.

GATES

This function comes in a wide variety of configurations. There are 2, 3, 4, or more inputs and 4 categories as follows:

AND: when all inputs go to "1" output will go to "1"

NAND: output will be "1" except when all inputs go to "1"

OR: when any input goes to "1" output will be "1"


NOR: output will be "1" except when any input goes to "1"

NAND and **NOR** differ from **AND** and **OR** in that inversion has taken place. Refer to the following illustrations. (Note the small o at the input or output of some of the examples. This o indicates that inversion has taken place).

Gates can be connected to operate in a wide variety of applications other than those for which they were designed. Some applications are:

Free — running (astable) multivibrator; bi-stable (flip-flop); "One Shot" multivibrator; amplifier, dc and ac; audio mixers.

Occasionally the time arises when the hobbyist-experimenter needs something in the way of gates other than what he has or what is available. For example, you need a 3-input gate and you have a 4-input gate; simply ground one input. Ground two inputs to obtain a 2-input gate. If you have a dual 2-input gate, such as the HEP-580, and you need a 4-input gate, tie pins 6 and 7 together and this becomes the output; inputs are then on pins 1, 2, 3, and 5.

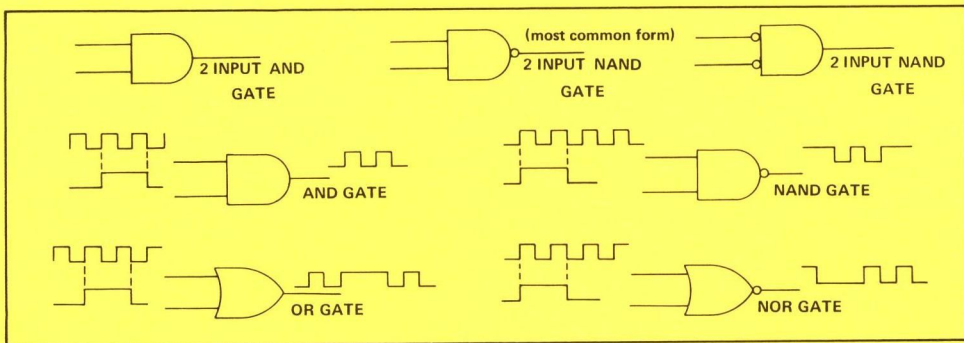

AMPLIFIER


In digital work it is referred to as a Buffer. Its original use is to increase "fan-in" or "fan-out" capability. That is, the number of other units than can be connected in parallel to the

input (fan-in) or output (fan-out). By adding proper external biasing it is possible to connect this unit to LINEAR (audio-RF) usage.

FLIP-FLOP


There are a number of types of flip-flops available. As mentioned previously, a flip-flop (multivibrator) can be "made up" by cross connecting two gates. The R-S Flip-Flop is one

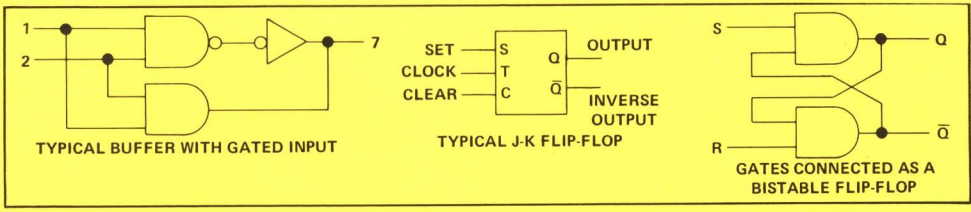example. The J-K Flip-Flop is similar but has the added function known as "clock input" shown as "T" on the logic block.




Fundamentally, flip-flops divide by two. By proper connection, division by 3,4,5 etc. can be obtained, using a few IC's as follows:

LOGIC DIAGRAMS

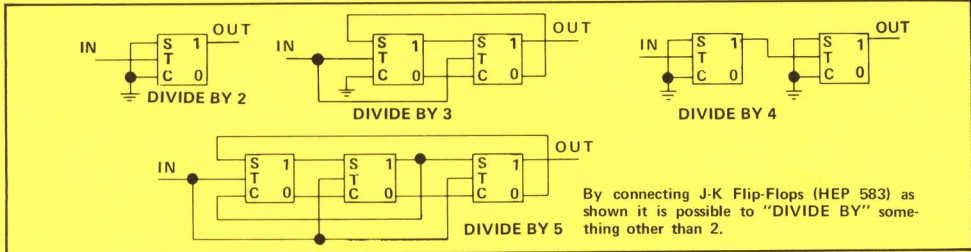

Schematic and logic diagrams of the HEP IC's that are contained in the HEK-1 Experimenters Kit and are used in the projects of this brochure are shown in the following illustrations:

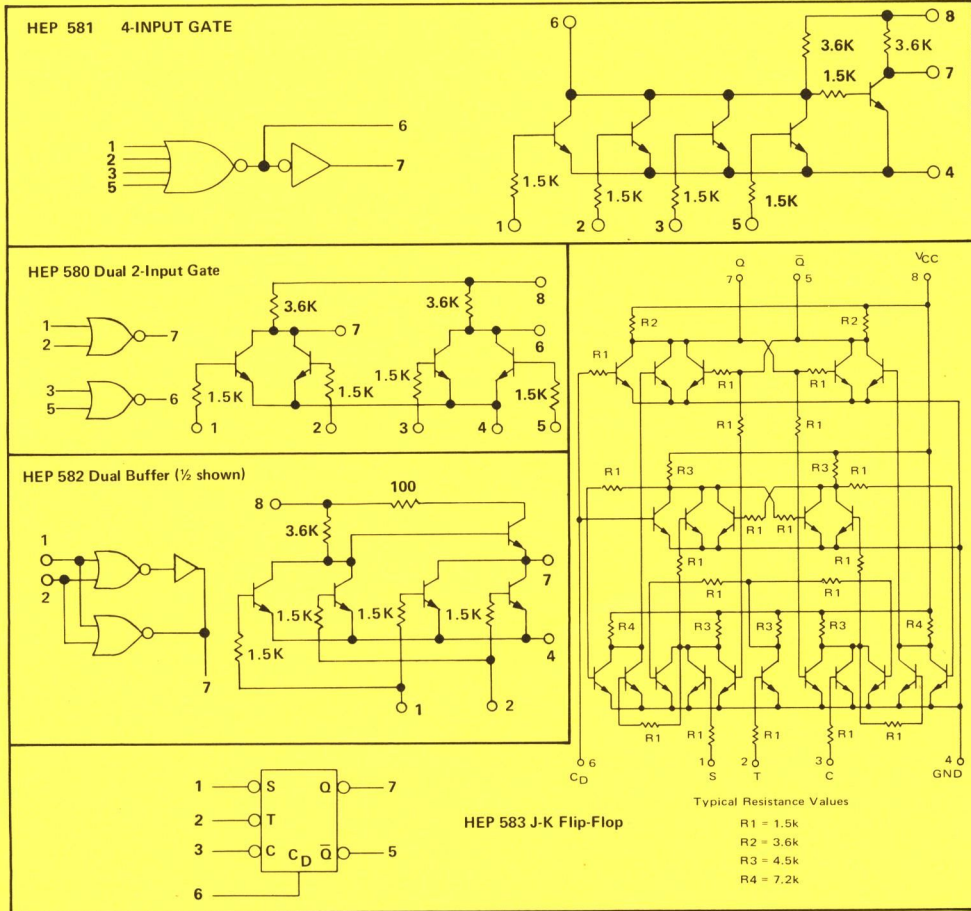


CKT. 1. ELECTRONIC SIREN

USES:
Burglar and intrusion alarms, automotive thefts and tamper alarms, toy sirens for bicycles.

FEATURES:
By slight changes in pot. setting — a wide variety of siren sounds can be obtained.

- PARTS LIST:**
- | | |
|--|--|
| Siren | Output Jack (if external amp is used) |
| 2 HEP 580 Dual 2-Input Gates | 2 HEP 454 IC Sockets |
| 5 680 Ω Resistors ¼ or ½ watt 10% | Vector Board and Terminals |
| 5 250 K or 100 K Potentiometers (trimmers) | AMPLIFIER |
| 2 50 μF Capacitors Electrolytic 10 Volts (or higher) | 1 1 meg Resistor ¼ or ½ watt 10% |
| 3 0.1 μF Capacitors, Disc Ceramic | 1 HEP 50 NPN Transistor |
| 1 ON-OFF Switch | 1 HEP 53 NPN Transistor |
| 9 Volt Battery (transistor radio) | 1 8 Ω Speaker 1½ to 2½ inches diameter |
| | 2 Transistor Sockets |

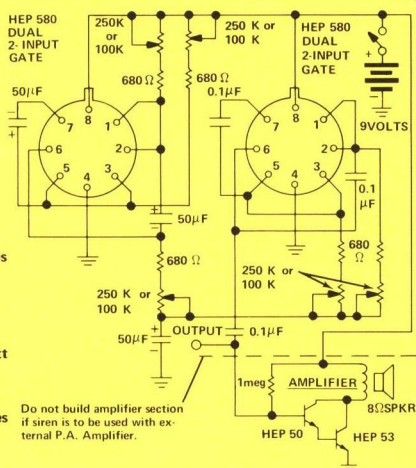

LINEAR IC'S

Linear IC's must be of particular interest to the TV-radio repair technician. Broadly speaking they are all amplifiers, the specific difference being in the power output, impedances, etc. For example, the HEP 592 is a complete stereo pre-amp, the only thing required

externally being the potentiometers. The HEP 590 can operate as an RF or IF stage. Experimentation with linear IC's is very straight forward and many circuits have been published that lend themselves very well to the HEP 590, 591, 592 and 593 devices.

IC CROSS REFERENCE FOR HOBBYIST EXPERIMENTERS

Type to be Replaced	See Note	HEP Replacement	Type to be Replaced	See Note	HEP Replacement	Type to be Replaced	See Note	HEP Replacement
CA3002		590	MC811F	2	581	SW303T		553
CA3003		590	MC814G		584	SW304F	2	554
CA3004		590	MC814F	2	584	SW304T		554
CA3013		591	MC817P	1	570	SW306F	2	556
CA3014		591	MC824P	1	570	SW306T		556
MC303G		553	MC876P	1	572	SW308F	2	558
MC303F	2	553	MC881G	1	582	SW308T		558
MC304G		554	MC882G	1	583	SW353F	2	553
MC304F	2	554	MC890P	1	572	SW353T		553
MC306G		556	MC899P	1	571	SW354F	2	554
MC306F	2	556	MC910G	1	580	SW354T		554
MC308G		558	MC910F	1, 2	580	SW356F	2	556
MC308F	2	558	MC911G	1	581	SW356T		556
MC353G		553	MC911F	1, 2	581	SW358F	2	558
MC353F	2	553	MC914G	1	584	SW358T		558
MC354F		554	MC914F	2	584	U3F991129X	2	581
MC354F	2	554	MC981G	1	582	U3F991421X	2	584
MC356G		556	MC982G	1	583	U3F991422X	2	584
MC356F	2	556	MC1302G		592	U5B991021X		580
MC358G		558	MC1302P	2	592	U5B991029X		580
MC358F	2	558	MC1303P	2,3	592	U5B991129X		581
MC710G		580	MC1314G		591	U5B991421X		584
MC710F	2	580	MC1550G		590	U5B991422X		584
MC711G		581	MC1554G		593	U5B991429X		584
MC711F	2	581	PA713		590	U5B992329X	4	572
MC714G		584	PA7601		590	U5B992329X	3	583
MC714F	2	584	PL990029	4	571	U5F991121X	2	581
MC717P	3	570	PL991021	1	580	U5B770339X		590
MC724P		570	PL991029		580	U5D990029X	4	571
MC776P	3	572	PL991129		581	U5D990029X	3	582
MC781G		582	PL991429		584	WM1146T		590
MC782G		583	PL992329	4	572	μL900	4	571
MC790P		572	PL992329	3	583	μL911	3	581
MC799P		571	SN17810L	1	580	μL914	(4)	584 (570)
MC810G		580	SN17910L	1	580	μL923	4	572
MC810F	2	580	SN17811L	1	581			
MC811G		581	SW303F	2	553			

Note 1: Temperature range is narrower.

Note 3: Milliwatt vs Medium power may require slight circuit value variations to optimize performance.

Note 2: Case Difference

Note 4: Plastic replaces 2 metal units (Case Difference)

CKT. 2.

SIGNAL INJECTOR AUDIO SIGNAL PROBE FOR SIGNAL INJECTION IN TESTING AM RECEIVERS OR AUDIO AMPLIFIERS

SPECIFICATIONS:


Output voltage variable 1 to 7 V
peak-to-peak, 1300 cps tone.
Battery drain at 9. Vdc =5.5mA.

PARTS LIST:

- 1 IC-1 = HEP-580
- 1 100 K Ω ½ watt resistors (R₁ & R₂)
- R₃ = 50 K Ω potentiometer s/switch linear taper (output control)

- C₁ = .001 μ F 25 V capacitor
 - C₂ = .1 μ F 25 V capacitor
 - C₃ = .1 μ F 600 V capacitor
 - B₁ = 9 V battery
 - R₄ = 1 K Ω ½ watt resistor
- Misc = wire solder etc.

NOTE: Frequency of tone may be raised or lowered by lowering or raising the value of C₁.

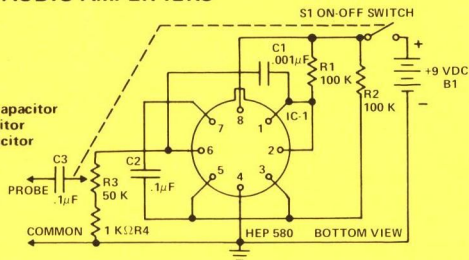

CKT. 3.

AUDIO SIGNAL GENERATOR

USES:

General Audio Testing


FEATURES:

Output Adjustable From 0 Volts to Approximately 2 Volts PK-PK. Sine Wave Output Fixed Frequency Approximately 1000 CPS.

PARTS LIST:

- 1 HEP 580 Dual 2-Input Gate
- 3 0.1 μ F Capacitors Disc Ceramic
- 1 1 μ F Capacitor Electrolytic 10 Volts (or higher)

- 2 15 K Resistors ¼ or ½ watt 10%
- 1 220 Ω Resistors ¼ or ½ watt 10%
- 1 1.8 K Resistors ¼ or ½ watt 10%
- 1 ON-OFF Switch (may be part of Gain Adjust).
- 1 50 K Potentiometer (audio taper)
- 1 9 Volt Transistor Radio Battery
- Output Jacks (as desired)
- Vector Board and Terminals
- 1 HEP 454 IC Socket

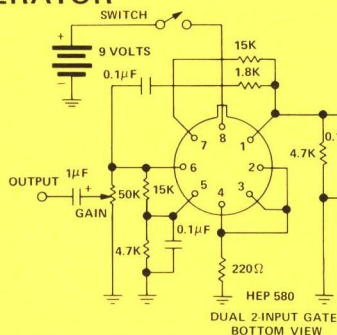

CKT. 4.

4 CHANNEL PREAMP MIXER

MIX 4 LOW LEVEL AUDIO SIGNALS FOR ONE OUTPUT


SPECIFICATIONS:

At 0.25 V pk-to-pk input, output is constant 4.5 V pk-to-pk 20 Hz to 1.MHz \pm 1 db. (input voltage must not exceed 0.25 V pk-to-pk over the frequency range specified) Current drain @ 9 Vdc = 3.0 MA.

PARTS REQUIRED:

- 1 HEP 580 IC
- 1 HEP 454 IC socket
- R₁ R₂ R₃ R₄ 330 K Ω resistors ½ watt
- C₁, C₂, C₃, C₄, C₅, 10 μ FD 10 V electrolytics
- S1= Spst switch
- 9 V Power source or battery

NOTE 1. Parts shown in dotted lines may be added for individual input level control, to maintain input voltage under 0.25 Vac rms.

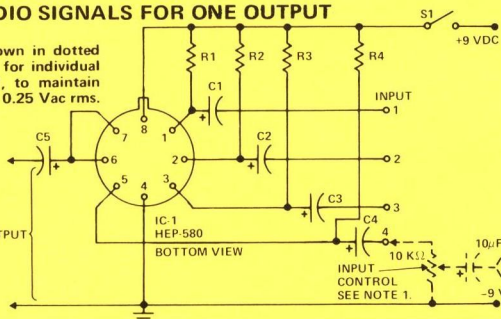

CKT. 5.

SQUARING AMP (SINE TO SQUARE WAVE CONVERTER) USING HEP 581 4 INPUT OR/NOR GATE MW MRTL

SPECIFICATIONS:


2.0 to 10.0 Vac sine wave input produces symmetrical square wave output 2. Vac peak-to-peak maximum. DC to 1 MHz current drain 3.5 MA at 9 Vdc.

SUGGESTED APPLICATION:
Test Hi-Fi amplifier frequency response in conjunction with oscilloscope.

NOTE: Pin 4 connected to CASE

PARTS REQUIRED:

- IC1 1 Hep 581
- R₁ 33 K resistor
- R₂ 100 K pot with switch (SW-1)
- R₃ - 2200 Ω
- C₁ & C₂ 10 μ F electrolytics at 10 Vdc
- 1 HEP 454 IC socket
- 9 V battery or power supply

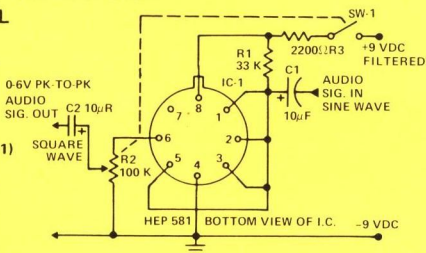

CKT. 6.

HEP WIDE BAND PREAMPLIFIER USING HEP 580 DUAL 2 INPUT NOR GATE

SPECIFICATIONS:

With 9.0 Vdc supply and .01 Vac P-P input. Output is approx. 1 volt = 10 Hz to 1 MHz. Current drain = .2 ma. Gain factor over specified bandwidth = 100.

PARTS REQUIRED FOR WIDE BAND AMP.

IC-1 = HEP 580

C₁ C₂ = 10 MFD 10 volt electrolytics


R₁ = 1 meg ¼ or ½ watt resistor
R₂ 22 K ½ or ¼ watt. HEP 454 IC socket

9 V Battery or power source

Misc wire, solder etc.

SW-1 ON-OFF Switch

NOTE: Pin 4 connected to case

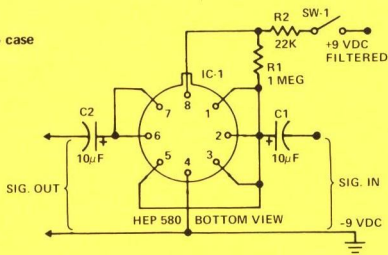

SUGGESTED APPLICATIONS

Oscilloscope preamp
Microphone preamp
Phonograph preamp
Hearing Aid preamp
etc.

May also be used as a stereo (2 channel) Pre-amp or a 2 or 4 channel mixer. Please refer to the IC Chip schematic for input and output connections.

CKT. 7.

PRECISION TACHOMETER

USES:

Tachometer can be used on automobile, boat, motorcycle, etc.


FEATURES

Very flexible circuit — range and number of cylinders — compensated for by 1 adjustment.

PARTS LIST:

- 1 HEP 580 Dual z-Input Gate
- 1 HEP Z0412 Zener Diode (9.1V)
- 1 330 Ω ½ watt 10% Resistor
- 2 10 K ¼ or ½ watt 10% Resistor
- 1 680 Ω ¼ or ½ watt 10% Resistor
- 2 1 K ½ or ¼ watt 10% Resistor
- 1 100 µF Capacitor Electrolyc 15 Volts (or higher)
- 1 50 µF Capacitor Electrolyc 10 Volts (or higher)
- 1 0.01 µF Capacitor Disc Ceramic
- 1 0.1 µF Capacitor Disc Ceramic

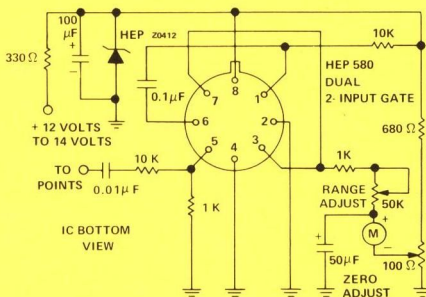- 1 100 Ω Potentiometer (trimmer)
- 1 50K Potentiometer Linear (range adjust)
- 1 50 µA meter
- Vector Board and Terminals
- 1 HEP 454 IC Socket



OPERATION FOR CALIBRATION

Connect lines to ground, 12 Volts, and points with engine turned off but ignition switch "on". Zero meter with Zero Adjust. To set range — check auto speed using a tach from a service station or garage.

(Range maximum can be whatever you desire. And calibrate the rest of the scale accordingly.) As an arbitrary adjustment, most automobiles idle at about 600 RPM — with engine idling — adjust Range pot until needle is in approximately the 600 RPM position.

CKT. 8.

XTAL CONTROLLED FREQUENCY SOURCE SQUARE WAVE

SPECIFICATIONS:

Accurate frequency source of 100 or 50 kHz square wave signals for test purposes or markers for communications receivers. Operates from 5 to 15 Vdc at 9.0 Vdc current. Drain is 5.5 MA. Voltage output at "A" or "B" is 1.0 volts peak-to-peak at 9 Vdc power source.

PARTS LIST:

- 1 HEP 580 Dual 2 input GATE
- 1 HEP 583 J-K flip-flop
- R₁ & R₂ 100 K Ω resistors ½ watt
- X₁ 100 kHz crystal
- C₁ .001 µF cap
- C₂ & C₃ .1 µF cap
- 2 HEP 454 IC sockets
- 1 XTAL socket
- R₃ 1 K Ω resistor ½ watt
- Misc: Solder wire etc.
- 9 V Battery or power supply
- S1 Spst switch

